

# ConceptTest PowerPoints

## Chapter 19

### *Physics: Principles with Applications, 6<sup>th</sup> edition*

Giancoli

© 2005 Pearson Prentice Hall


This work is protected by United States copyright laws and is provided solely for the use of instructors in teaching their courses and assessing student learning. Dissemination or sale of any part of this work (including on the World Wide Web) will destroy the integrity of the work and is not permitted. The work and materials from it should never be made available to students except by instructors using the accompanying text in their classes. All recipients of this work are expected to abide by these restrictions and to honor the intended pedagogical purposes and the needs of other instructors who rely on these materials.

## ConceptTest 19.1a

## Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**. What is the potential difference across each resistor?

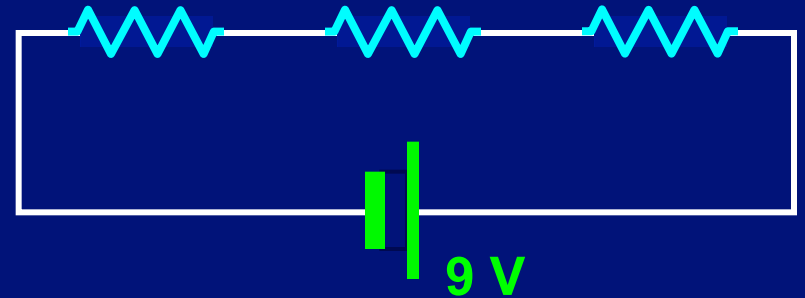- 1) 12 V
- 2) zero
- 3) 3 V
- 4) 4 V
- 5) you need to know the actual value of  $R$



## ConceptTest 19.1a

## Series Resistors I

Assume that the voltage of the battery is **9 V** and that the three resistors are **identical**. What is the potential difference across each resistor?

1) 12 V


2) zero

3) 3 V

4) 4 V

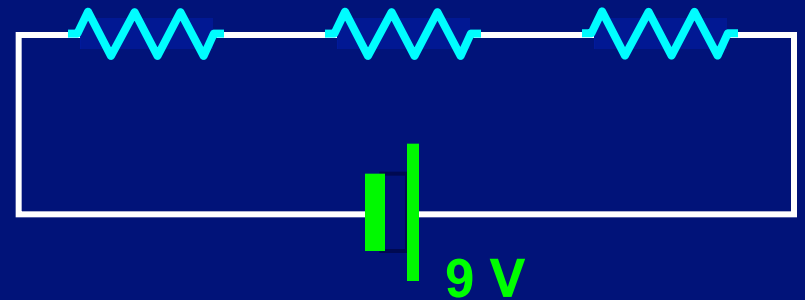5) you need to know the actual value of  $R$

Since the resistors are all **equal**, the voltage will drop **evenly** across the 3 resistors, with  $1/3$  of 9 V across each one. So we get a **3 V drop** across each.



**Follow-up:** What would be the potential difference if  $R = 1 \Omega, 2 \Omega, 3 \Omega$

## ConceptTest 19.1b

## Series Resistors II

In the circuit below, what is the voltage across  $R_1$ ?

- 1) 12 V
- 2) zero
- 3) 6 V
- 4) 8 V
- 5) 4 V



## ConceptTest 19.1b

## Series Resistors II

In the circuit below, what is the voltage across  $R_1$ ?

1) 12 V


2) zero

3) 6 V

4) 8 V

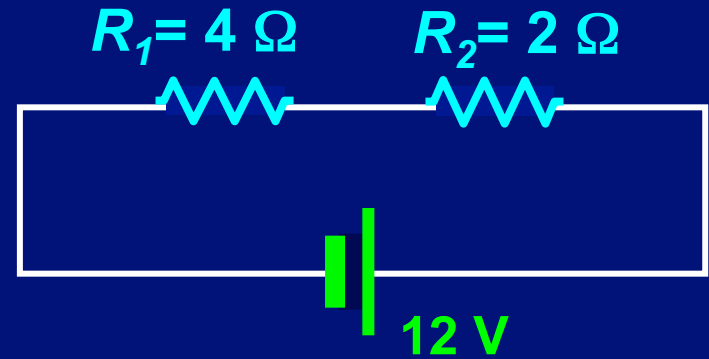5) 4 V

The voltage drop across  $R_1$  has to be twice as big as the drop across  $R_2$ . This means that  $V_1 = 8 \text{ V}$  and  $V_2 = 4 \text{ V}$ . Or else you could find the current  $I = V/R = (12 \text{ V})/(6 \Omega) = 2 \text{ A}$ , then use Ohm's Law to get voltages.




Follow-up: What happens if the voltage is doubled?

## ConceptTest 19.2a

## Parallel Resistors I

In the circuit below, what is the current through  $R_1$ ?

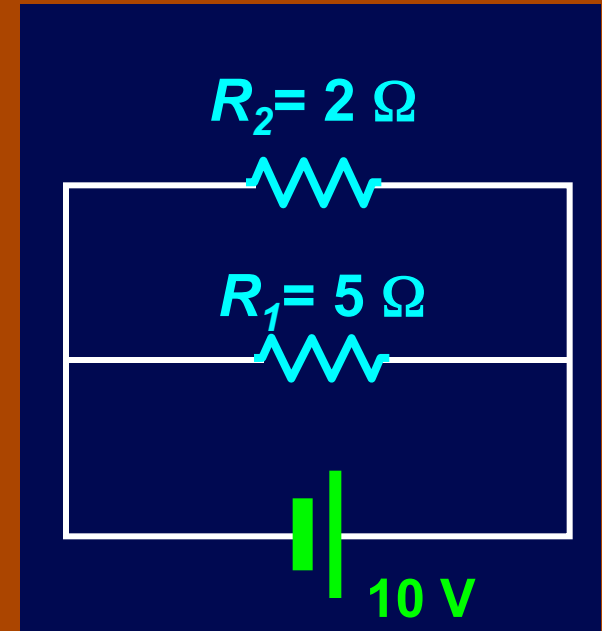- 1) 10 A
- 2) zero
- 3) 5 A
- 4) 2 A
- 5) 7 A



## ConceptTest 19.2a

## Parallel Resistors I

In the circuit below, what is the current through  $R_1$ ?

1) 10 A


2) zero

3) 5 A

4) 2 A

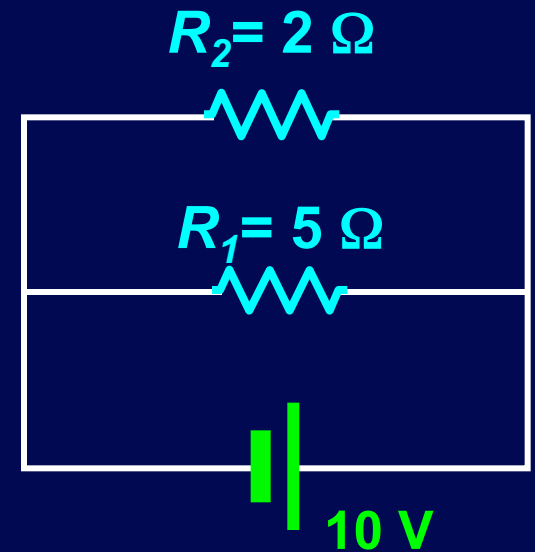5) 7 A

The **voltage** is the **same** (10 V) across each resistor because they are in parallel. Thus, we can use Ohm's Law,  $V_1 = I_1 R_1$  to find the current  $I_1 = 2 \text{ A}$ .




Follow-up: What is the total current through the battery?

## ConceptTest 19.2b

## Parallel Resistors II

Points P and Q are connected to a battery of fixed voltage. As more resistors  $R$  are added to the parallel circuit, what happens to the **total current** in the circuit?

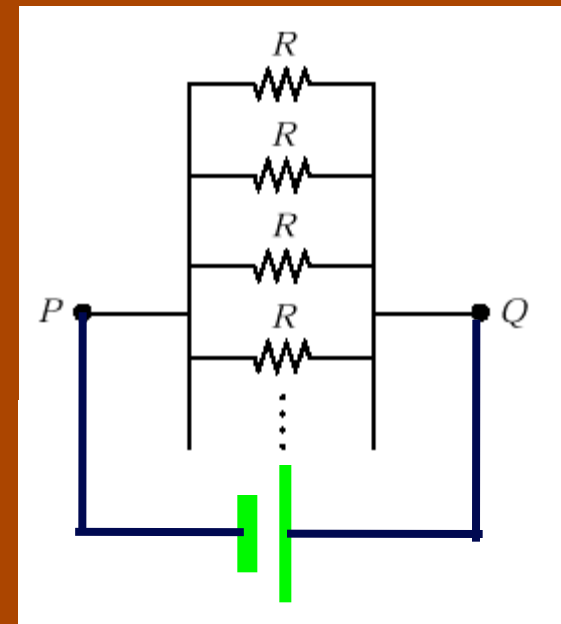- 1) increases
- 2) remains the same
- 3) decreases
- 4) drops to zero






## ConceptTest 19.2b

## Parallel Resistors II

Points P and Q are connected to a battery of fixed voltage. As more resistors  $R$  are added to the parallel circuit, what happens to the **total current** in the circuit?

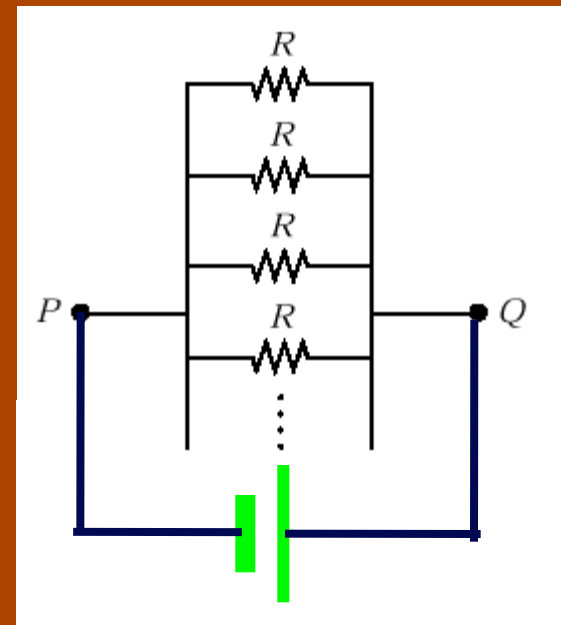- 1) increases
- 2) remains the same
- 3) decreases
- 4) drops to zero

As we add parallel resistors, the overall **resistance of the circuit drops**. Since  $V = IR$ , and  $V$  is held constant by the battery, when **resistance decreases**, the **current must increase**.




**Follow-up:** What happens to the current through each resistor?

## ConceptTest 19.3a

## Short Circuit

Current flows through a lightbulb. If a wire is now connected across the bulb, what happens?

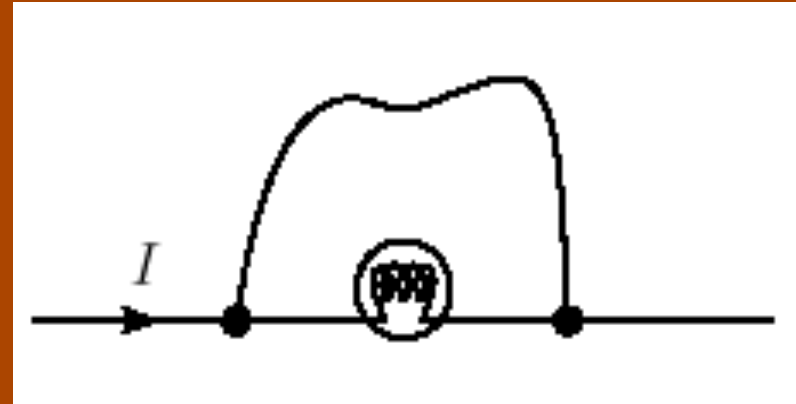- 1) all the current continues to flow through the bulb
- 2) half the current flows through the wire, the other half continues through the bulb
- 3) all the current flows through the wire
- 4) none of the above




## ConceptTest 19.3a

## Short Circuit

Current flows through a lightbulb. If a wire is now connected across the bulb, what happens?

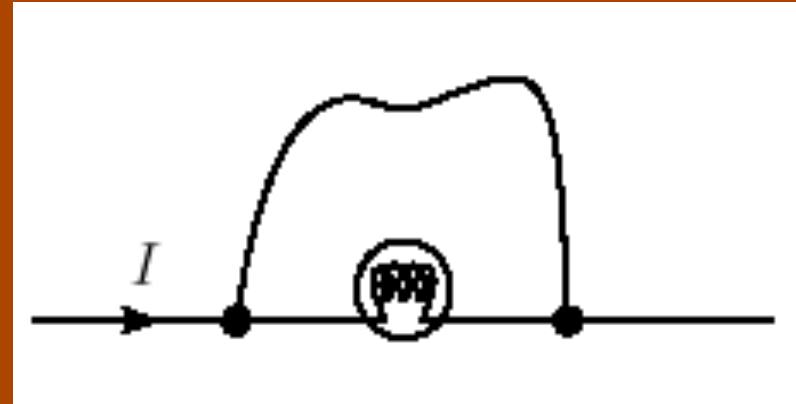- 1) all the current continues to flow through the bulb
- 2) half the current flows through the wire, the other half continues through the bulb
- 3) all the current flows through the wire
- 4) none of the above

The current divides based on the ratio of the resistances. If one of the resistances is **zero**, then **ALL** of the current will flow through that path.




**Follow-up:** Doesn't the wire have SOME resistance?

## ConceptTest 19.4a

## Circuits I

The lightbulbs in the circuit below are identical with the same resistance  $R$ . Which circuit produces more light? (brightness  $\iff$  power)

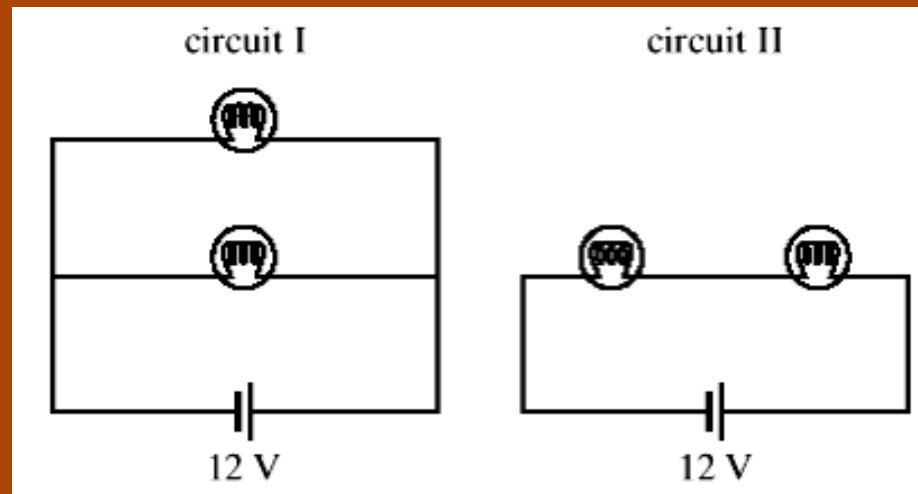- 1) circuit 1
- 2) circuit 2
- 3) both the same
- 4) it depends on  $R$



## ConceptTest 19.4a


## Circuits I

The lightbulbs in the circuit below are identical with the same resistance  $R$ . Which circuit produces more light? (brightness  $\iff$  power)


- 1) circuit 1
- 2) circuit 2
- 3) both the same
- 4) it depends on  $R$

In #1, the bulbs are in parallel, lowering the total resistance of the circuit. Thus, circuit #1 will draw a higher current, which leads to more light, because  $P = IV$ .

circuit I

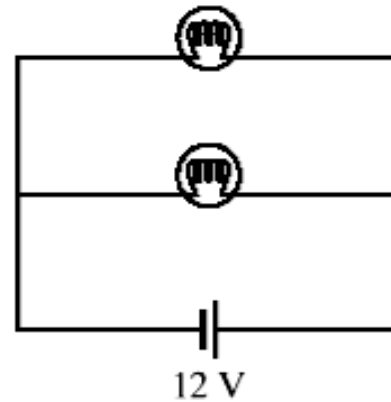

circuit II

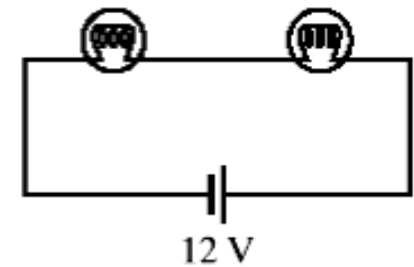


## ConcepTest 19.4b

## Circuits II

The three lightbulbs in the circuit all have the **same resistance of  $1\ \Omega$** . By how much is the **brightness of bulb B** greater or smaller than the **brightness of bulb A**? (brightness  $\iff$  power)

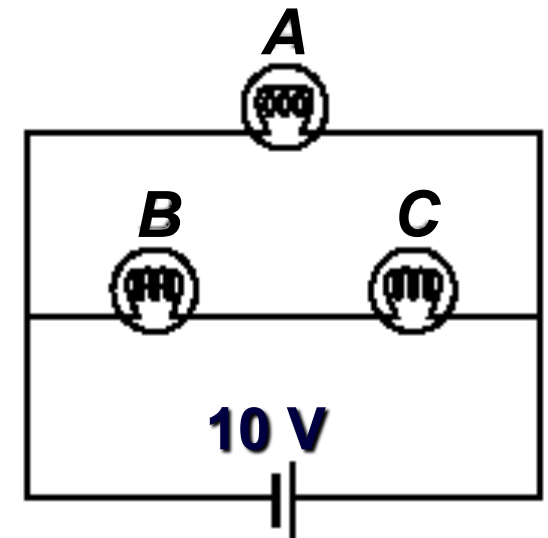- 1) twice as much
- 2) the same
- 3)  $1/2$  as much
- 4)  $1/4$  as much
- 5) 4 times as much



## ConcepTest 19.4b

## Circuits II


The three light bulbs in the circuit all have the **same resistance of  $1 \Omega$** . By how much is the **brightness of bulb B** greater or smaller than the **brightness of bulb A**? (brightness  $\iff$  power)

- 1) twice as much
- 2) the same
- 3) 1/2 as much
- 4) 1/4 as much
- 5) 4 times as much

We can use  $P = V^2/R$  to compare the power:

$$P_A = (V_A)^2/R_A = (10 \text{ V})^2/1 \Omega = 100 \text{ W}$$
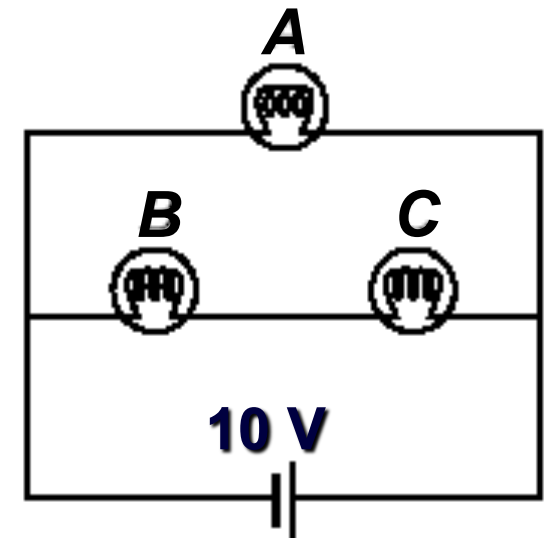
$$P_B = (V_B)^2/R_B = (5 \text{ V})^2/1 \Omega = 25 \text{ W}$$




**Follow-up:** What is the total current in the circuit?

## ConceptTest 19.5a

## More Circuits I

What happens to the voltage across the resistor  $R_1$  when the switch is closed? The voltage will:

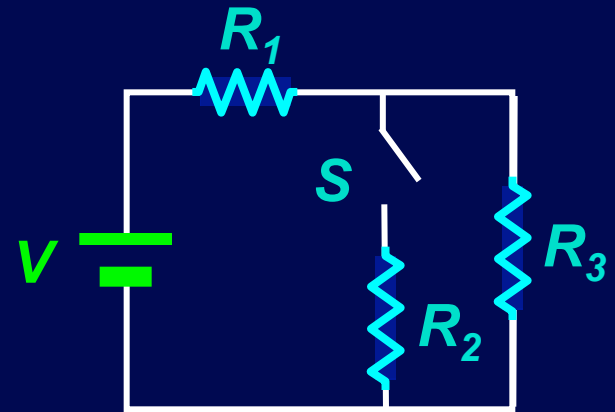- 1) increase
- 2) decrease
- 3) stay the same






## ConceptTest 19.5a

## More Circuits I

What happens to the voltage across the resistor  $R_1$  when the switch is closed? The voltage will:

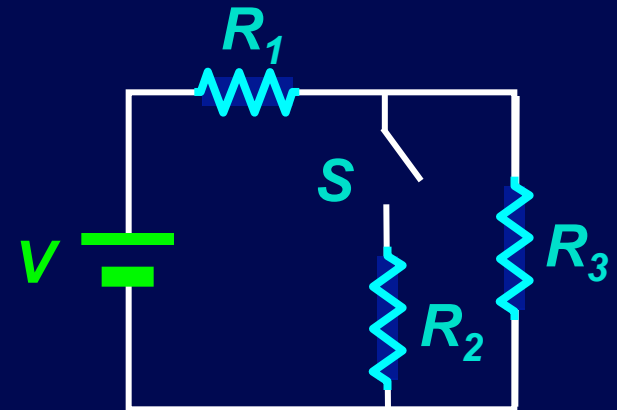- 1) increase
- 2) decrease
- 3) stay the same

With the switch closed, the addition of  $R_2$  to  $R_3$  decreases the equivalent resistance, so the current from the battery increases. This will cause an increase in the voltage across  $R_1$ .




**Follow-up:** What happens to the current through  $R_3$ ?

## ConceptTest 19.5b

## More Circuits II

What happens to the voltage across the resistor  $R_4$  when the switch is closed?

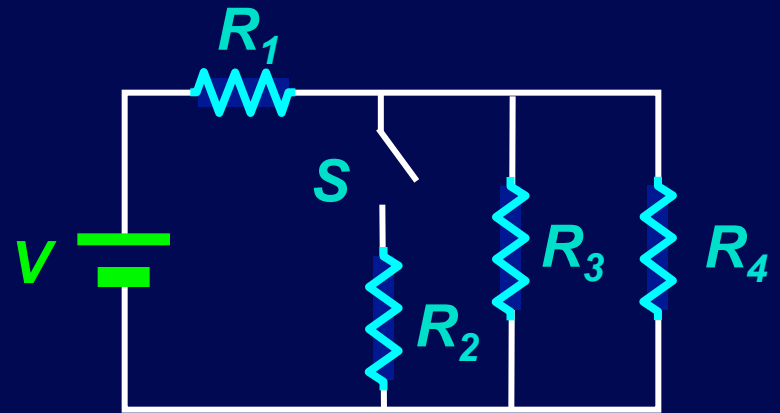- 1) increases
- 2) decreases
- 3) stays the same



## ConceptTest 19.5b

## More Circuits II


What happens to the voltage across the resistor  $R_4$  when the switch is closed?

1) increases

2) decreases

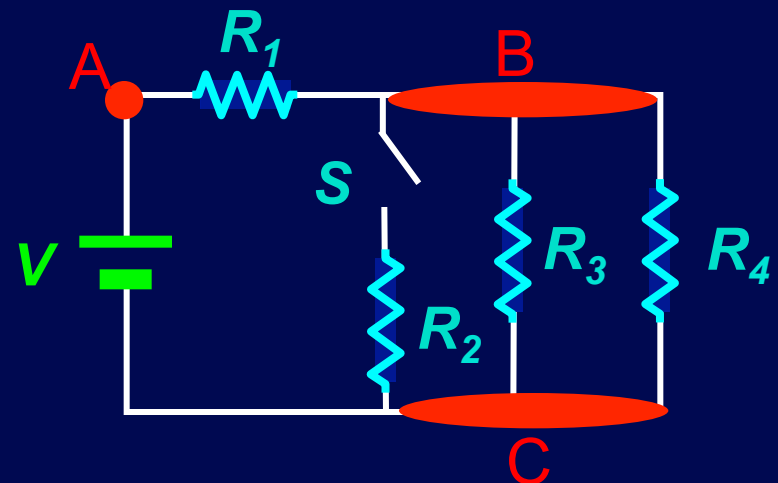3) stays the same

We just saw that closing the switch causes an increase in the voltage across  $R_1$  (which is  $V_{AB}$ ). The voltage of the battery is constant, so if  $V_{AB}$  increases, then  $V_{BC}$  must decrease!




Follow-up: What happens to the current through  $R_4$ ?

## ConceptTest 19.6

Which resistor has the greatest current going through it? Assume that all the resistors are equal.

## Even More Circuits

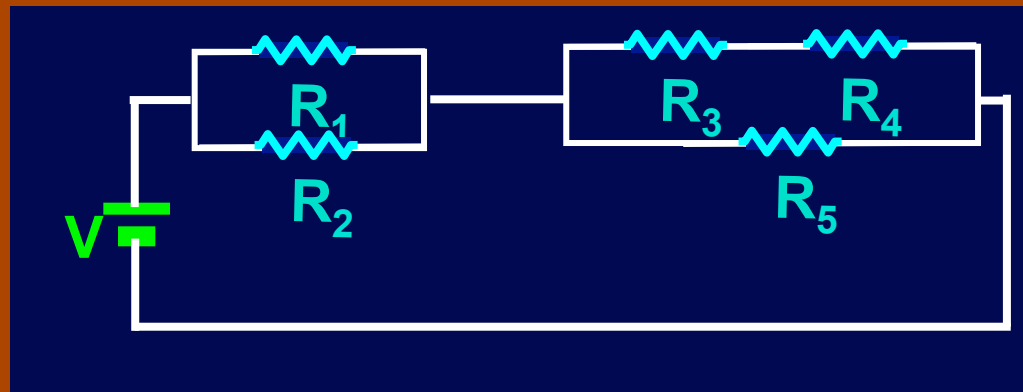- 1)  $R_1$
- 2) both  $R_1$  and  $R_2$  equally
- 3)  $R_3$  and  $R_4$
- 4)  $R_5$
- 5) all the same




## ConceptTest 19.6

Which resistor has the greatest current going through it? Assume that all the resistors are equal.

## Even More Circuits

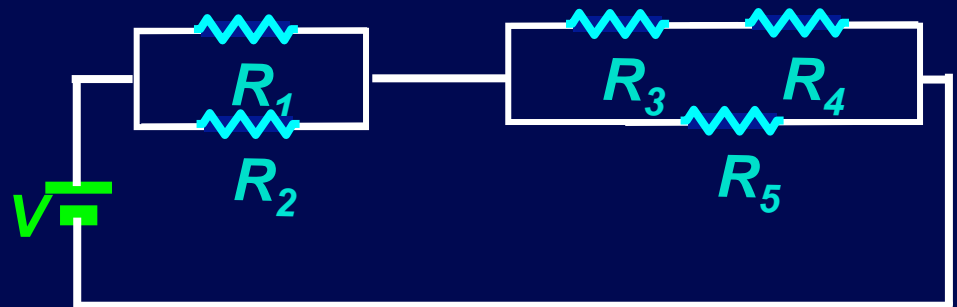- 1)  $R_1$
- 2) both  $R_1$  and  $R_2$  equally
- 3)  $R_3$  and  $R_4$
- 4)  $R_5$
- 5) all the same

The same current must flow through left and right combinations of resistors. On the LEFT, the current splits equally, so  $I_1 = I_2$ . On the RIGHT, more current will go through  $R_5$  than  $R_3 + R_4$  since the branch containing  $R_5$  has less resistance.




Follow-up: Which one has the smallest voltage drop?

## ConceptTest 19.7

## Junction Rule

What is the current in branch P?

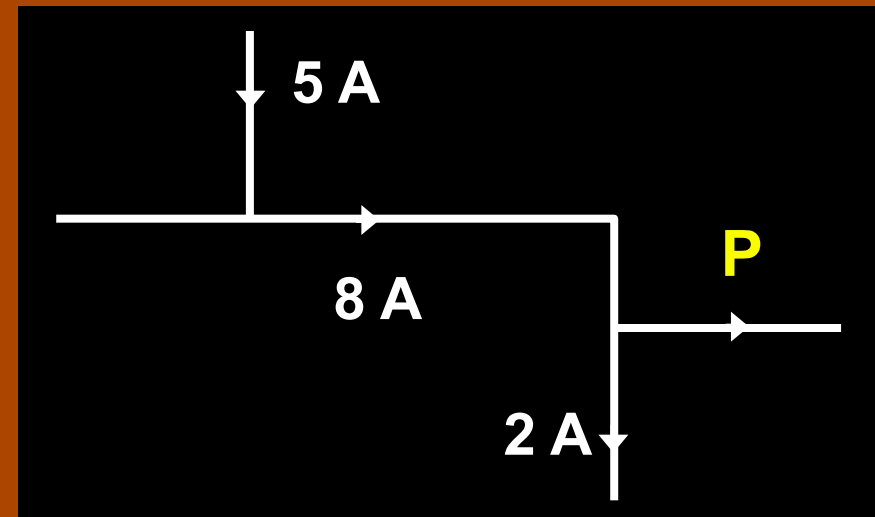- 1) 2 A
- 2) 3 A
- 3) 5 A
- 4) 6 A
- 5) 10 A



## ConceptTest 19.7

What is the current in branch P?

1) 2 A

2) 3 A


3) 5 A

4) 6 A

5) 10 A
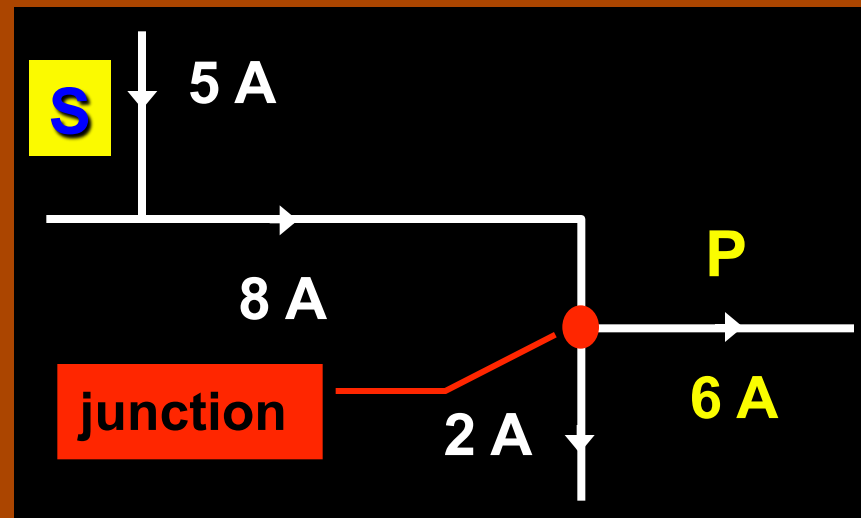
## Junction Rule

The current entering the junction in **red** is 8 A, so the current leaving must also be 8 A. **One exiting branch has 2 A**, so the other branch (at P) must have 6 A.




## ConceptTest 19.8

## Kirchhoff's Rules

The lightbulbs in the circuit are **identical**. When the switch is closed, what happens?

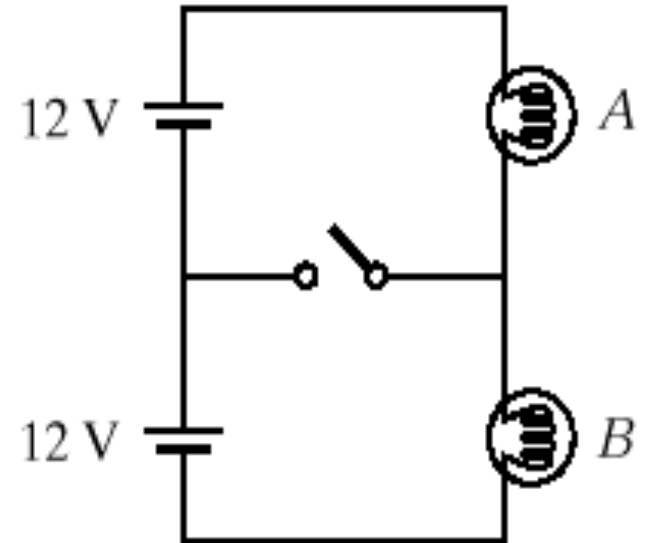- 1) both bulbs go out
- 2) intensity of both bulbs increases
- 3) intensity of both bulbs decreases
- 4) A gets brighter and B gets dimmer
- 5) nothing changes





## ConceptTest 19.8


## Kirchhoff's Rules

The lightbulbs in the circuit are **identical**. When the switch is closed, what happens?

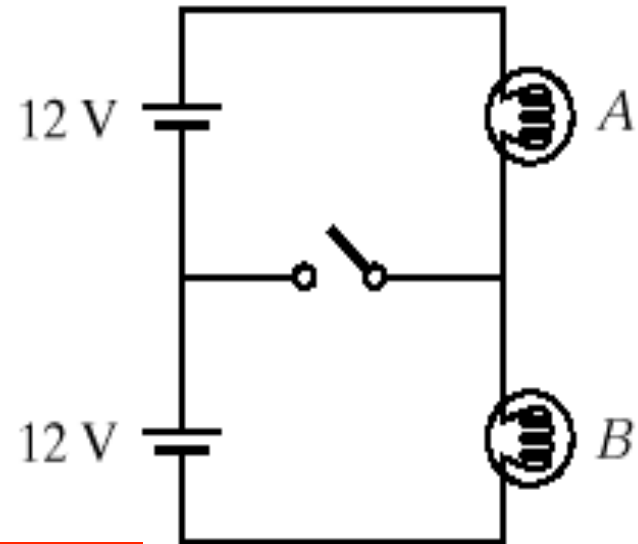- 1) both bulbs go out
- 2) intensity of both bulbs increases
- 3) intensity of both bulbs decreases
- 4) A gets brighter and B gets dimmer
- 5) nothing changes

When the switch is open, the point between the bulbs is at 12 V. But so is the point between the batteries. If there is no potential difference, then no current will flow once the switch is closed!! Thus, nothing changes.

**Follow-up:** What happens if the bottom battery is replaced by a 24 V battery?




24 V

## ConceptTest 19.9

An ammeter  $A$  is connected between points  $a$  and  $b$  in the circuit below, in which the four resistors are **identical**. The current through the ammeter is:

## Wheatstone Bridge

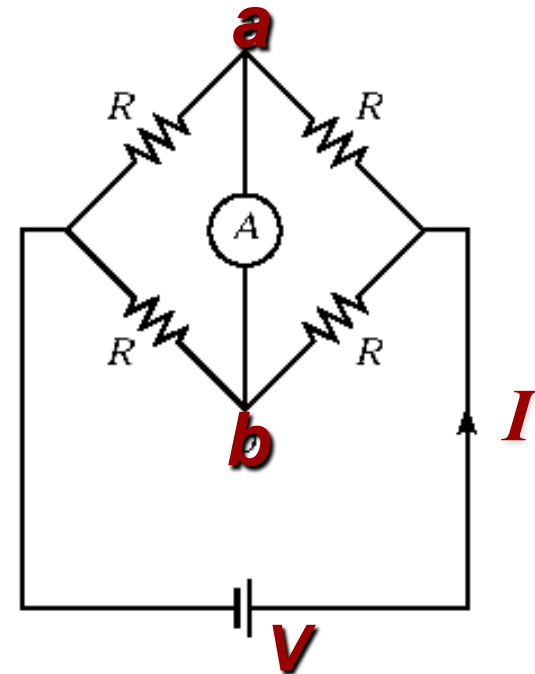- 1)  $I$
- 2)  $I/2$
- 3)  $I/3$
- 4)  $I/4$
- 5) zero




## ConceptTest 19.9

An ammeter  $A$  is connected between points  $a$  and  $b$  in the circuit below, in which the four resistors are **identical**. The current through the ammeter is:

## Wheatstone Bridge

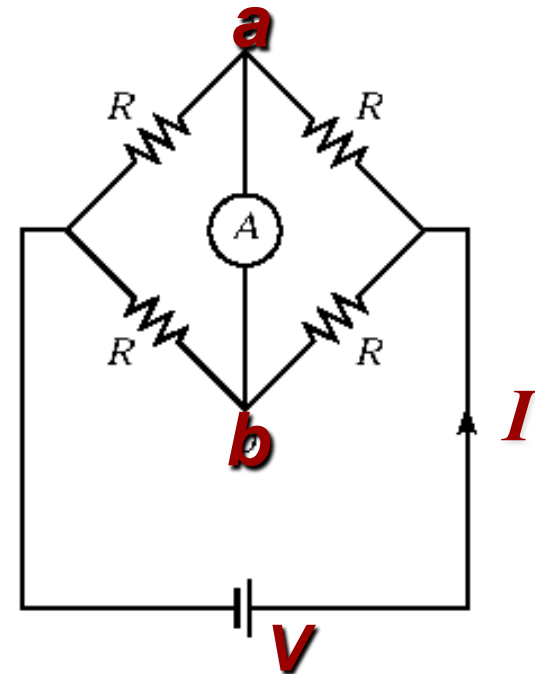- 1)  $I$
- 2)  $I/2$
- 3)  $I/3$
- 4)  $I/4$
- 5) **zero**

Since all resistors are identical, the voltage drops are the same across the upper branch and the lower branch. Thus, the potentials at points  $a$  and  $b$  are also the same. Therefore, no current flows.



## ConceptTest 19.10

## More Kirchhoff's Rules

Which of the equations is valid for the circuit below?


1)  $2 - I_1 - 2I_2 = 0$

2)  $2 - 2I_1 - 2I_2 - 4I_3 = 0$

3)  $2 - I_1 - 4 - 2I_2 = 0$

4)  $I_3 - 4 - 2I_2 + 6 = 0$

5)  $2 - I_1 - 3I_3 - 6 = 0$

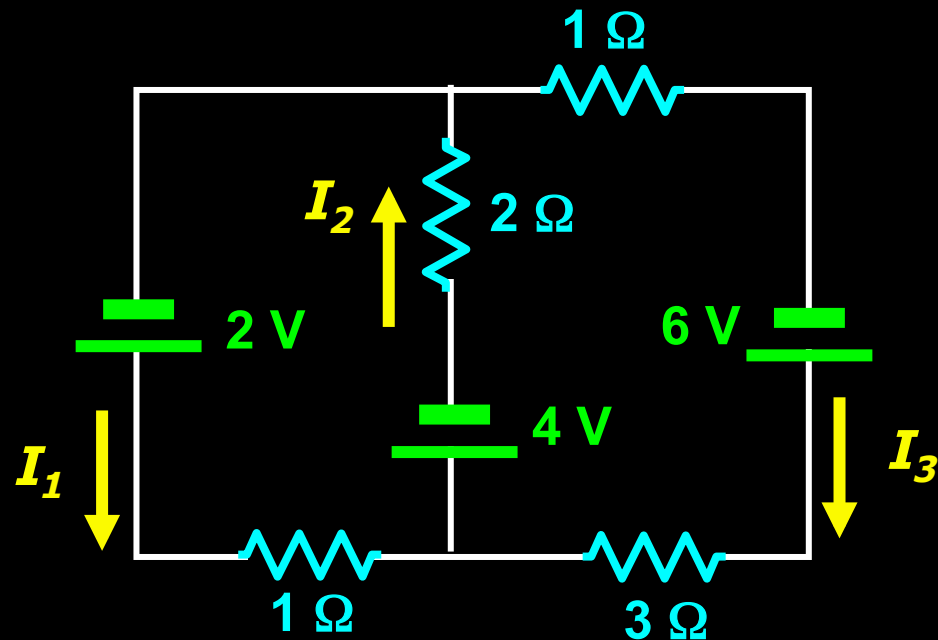

## ConceptTest 19.10

## More Kirchhoff's Rules

Which of the equations is valid for the circuit below?

1)  $2 - I_1 - 2I_2 = 0$


2)  $2 - 2I_1 - 2I_2 - 4I_3 = 0$

3)  $2 - I_1 - 4 - 2I_2 = 0$

4)  $I_3 - 4 - 2I_2 + 6 = 0$

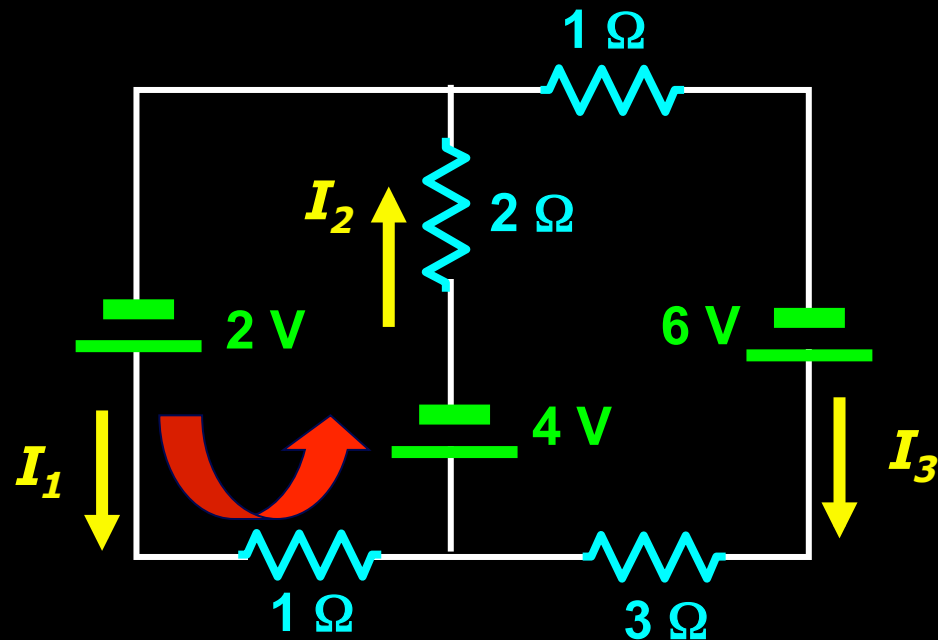5)  $2 - I_1 - 3I_3 - 6 = 0$

**Eqn. 3 is valid for the left loop:**  
The left battery gives +2V, then there is a drop through a  $1\Omega$  resistor with current  $I_1$  flowing. Then we go through the middle battery (but from + to - !), which gives -4V. Finally, there is a drop through a  $2\Omega$  resistor with current  $I_2$ .




## ConceptTest 19.11a

## Capacitors I

What is the equivalent capacitance,  $C_{eq}$ , of the combination below?

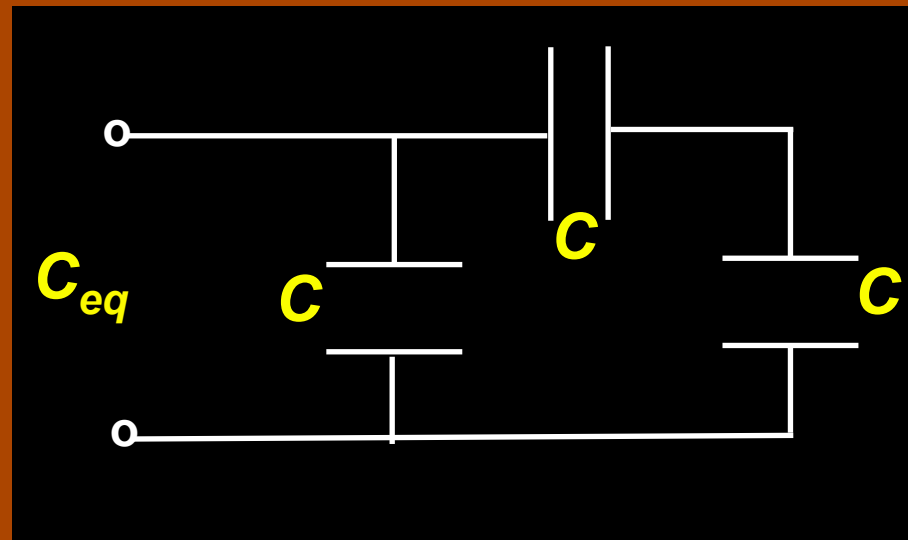- 1)  $C_{eq} = 3/2 C$
- 2)  $C_{eq} = 2/3 C$
- 3)  $C_{eq} = 3 C$
- 4)  $C_{eq} = 1/3 C$
- 5)  $C_{eq} = 1/2 C$



## ConceptTest 19.11a

## Capacitors I

What is the equivalent capacitance,  $C_{eq}$ , of the combination below?

1)  $C_{eq} = 3/2 C$


2)  $C_{eq} = 2/3 C$

3)  $C_{eq} = 3 C$

4)  $C_{eq} = 1/3 C$

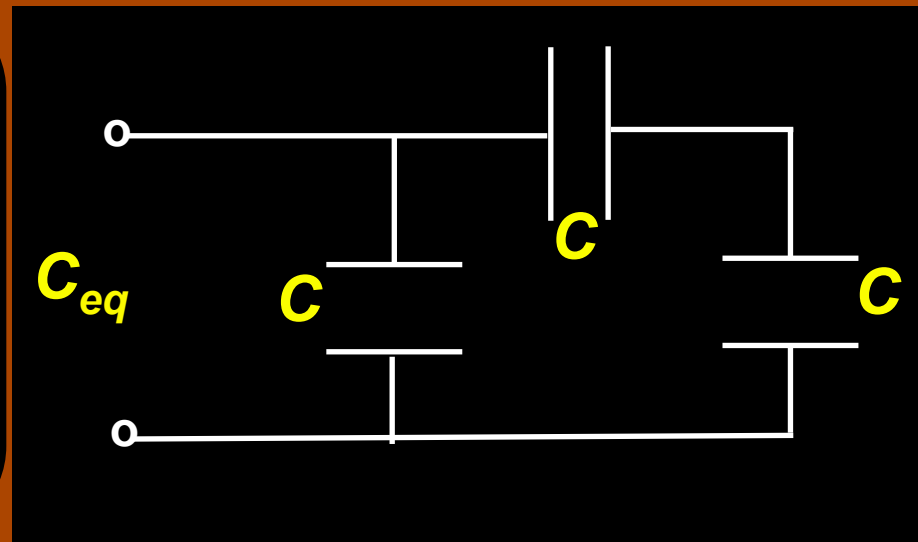5)  $C_{eq} = 1/2 C$

The 2 equal capacitors in **series** add up as **inverses**, giving  $1/2 C$ . These are **parallel** to the first one, which add up **directly**. Thus, the total equivalent capacitance is  $3/2 C$ .




## ConcepTest 19.11b

## Capacitors II

How does the voltage  $V_1$  across the first capacitor ( $C_1$ ) compare to the voltage  $V_2$  across the second capacitor ( $C_2$ )?

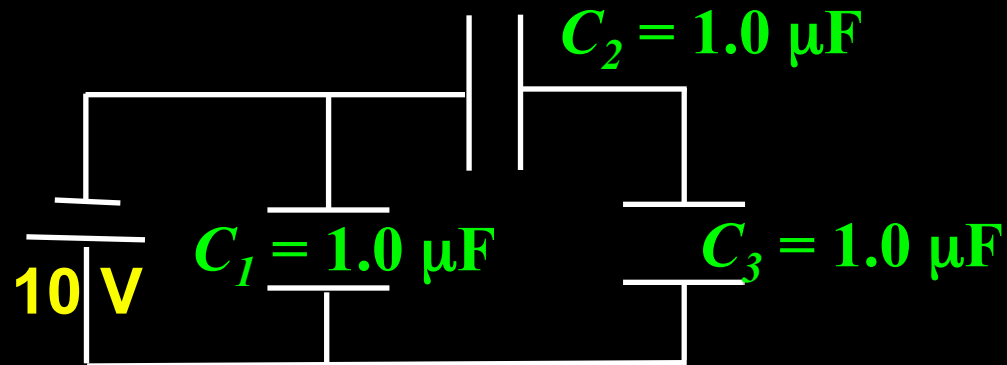- 1)  $V_1 = V_2$
- 2)  $V_1 > V_2$
- 3)  $V_1 < V_2$
- 4) all voltages are zero





## ConcepTest 19.11b

## Capacitors II

How does the voltage  $V_1$  across the first capacitor ( $C_1$ ) compare to the voltage  $V_2$  across the second capacitor ( $C_2$ )?


1)  $V_1 = V_2$

2)  $V_1 > V_2$

3)  $V_1 < V_2$

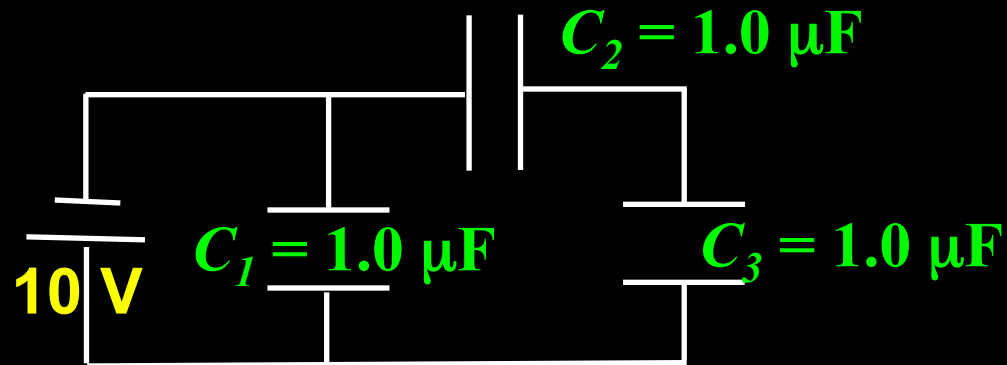4) all voltages are zero

The voltage across  $C_1$  is 10 V. The combined capacitors  $C_2+C_3$  are parallel to  $C_1$ . The voltage across  $C_2+C_3$  is also 10 V. Since  $C_2$  and  $C_3$  are in series, their voltages add. Thus the voltage across  $C_2$  and  $C_3$  each has to be 5 V, which is less than  $V_1$ .




Follow-up: What is the current in this circuit?

## ConceptTest 19.11c

## Capacitors III

How does the charge  $Q_1$  on the first capacitor ( $C_1$ ) compare to the charge  $Q_2$  on the second capacitor ( $C_2$ )?

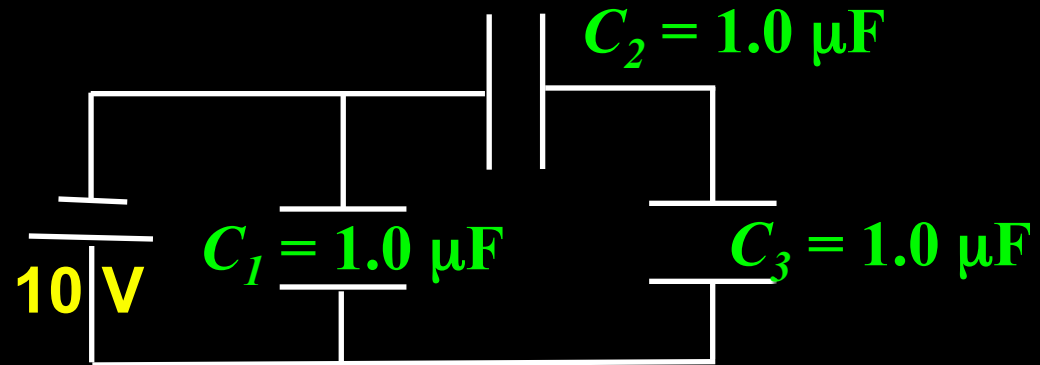- 1)  $Q_1 = Q_2$
- 2)  $Q_1 > Q_2$
- 3)  $Q_1 < Q_2$
- 4) all charges are zero



## ConcepTest 19.11c

## Capacitors III

How does the charge  $Q_1$  on the first capacitor ( $C_1$ ) compare to the charge  $Q_2$  on the second capacitor ( $C_2$ )?

1)  $Q_1 = Q_2$

2)  $Q_1 > Q_2$

3)  $Q_1 < Q_2$

4) all charges are zero

We already know that the voltage across  $C_1$  is 10 V and the voltage across  $C_2$  and  $C_3$  each is 5 V. Since  $Q = CV$  and  $C$  is the same for all the capacitors, then since  $V_1 > V_2$  therefore  $Q_1 > Q_2$ .

